

**VHDL Code
Simulation & Implementation
in ISE Xilinx**

Signed 4BIT Binary Multiplication

Mohammad Niknam

یک ضرب کننده بیتی علامت دار) و البته سنتز پذیر (را توصیف نمایید. توصیف باید استراکچرال و مبتنی بر جمع کننده ها باشد) که پیش از این توصیف کرده (همچنین یک تست بنچ برای ارزیابی صحت عملکرد بنویسید که خروجی را برای زوج ورودی هایی با علامت های متفاوت نمایش دهد) مثلاً یک بار دو عدد مثبت را در هم ضرب کند، بار دیگر یک عدد مثبت در منفی و بالاخره دو عدد منفی را.

1.6 SIGNED BINARY NUMBERS

Positive integers (including zero) can be represented as unsigned numbers. However, to represent negative integers, we need a notation for negative values. In ordinary arithmetic, a negative number is indicated by a minus sign and a positive number by a plus sign. Because of hardware limitations, computers must represent everything with binary digits. It is customary to represent the sign with a bit placed in the leftmost position of the number. The convention is to make the sign bit 0 for positive and 1 for negative.

It is important to realize that both signed and unsigned binary numbers consist of a string of bits when represented in a computer. The user determines whether the number is signed or unsigned. If the binary number is signed, then the leftmost bit represents the sign and the rest of the bits represent the number. If the binary number is assumed to be unsigned, then the leftmost bit is the most significant bit of the number. For example, the string of bits 01001 can be considered as 9 (unsigned binary) or as +9 (signed binary) because the leftmost bit is 0. The string of bits 11001 represents the binary equivalent of 25 when considered as an unsigned number and the binary equivalent of -9 when considered as a signed number. This is because the 1 that is in the leftmost position designates a negative and the other four bits represent binary 9. Usually, there is no confusion in interpreting the bits if the type of representation for the number is known in advance.

The representation of the signed numbers in the last example is referred to as the *signed-magnitude* convention. In this notation, the number consists of a magnitude and a symbol (+ or −) or a bit (0 or 1) indicating the sign. This is the representation of signed numbers used in ordinary arithmetic. When arithmetic operations are implemented in a computer, it is more convenient to use a different system, referred to as the *signed-complement* system, for representing negative numbers. In this system, a negative number is indicated by its complement. Whereas the signed-magnitude system negates a number by changing its sign, the signed-complement system negates a number by taking its complement. Since positive numbers always start with 0 (plus) in the leftmost position, the complement will always start with a 1, indicating a negative number. The signed-complement system can use either the 1's or the 2's complement, but the 2's complement is the most common.

As an example, consider the number 9, represented in binary with eight bits. +9 is represented with a sign bit of 0 in the leftmost position, followed by the binary equivalent of 9, which gives 00001001. Note that all eight bits must have a value; therefore, 0's are inserted following the sign bit up to the first 1. Although there is only one way to represent +9, there are three different ways to represent −9 with eight bits:

| | |
|---------------------------------------|----------|
| signed-magnitude representation: | 10001001 |
| signed-1's-complement representation: | 11110110 |
| signed-2's-complement representation: | 11110111 |

In signed-magnitude, −9 is obtained from +9 by changing only the sign bit in the leftmost position from 0 to 1. In signed-1's-complement, −9 is obtained by complementing all the bits of +9, including the sign bit. The signed-2's-complement representation of −9 is obtained by taking the 2's complement of the positive number, including the sign bit.

Table 1.3 lists all possible four-bit signed binary numbers in the three representations. The equivalent decimal number is also shown for reference. Note that the positive numbers in all three representations are identical and have 0 in the leftmost position. The signed-2's-complement system has only one representation for 0, which is always positive. The other two systems have either a positive 0 or a negative 0, something not encountered in ordinary arithmetic. Note that all negative numbers have a 1 in the leftmost bit position; that is the way we distinguish them from the positive numbers. With four bits, we can represent 16 binary numbers. In the signed-magnitude and the 1's-complement representations, there are eight positive numbers and eight negative numbers, including two zeros. In the 2's-complement representation, there are eight positive numbers, including one zero, and eight negative numbers.

The signed-magnitude system is used in ordinary arithmetic, but is awkward when employed in computer arithmetic because of the separate handling of the sign and the magnitude. Therefore, the signed-complement system is normally used. The 1's complement imposes some difficulties and is seldom used for arithmetic operations. It is useful as a logical operation, since the change of 1 to 0 or 0 to 1 is equivalent to a logical complement operation, as will be shown in the next chapter. The discussion of signed binary arithmetic that follows deals exclusively with the signed-2's-complement

Table 1.3
Signed Binary Numbers

| Decimal | Signed-2's Complement | Signed-1's Complement | Signed Magnitude |
|---------|--------------------------|--------------------------|---------------------|
| +7 | 0111 | 0111 | 0111 |
| +6 | 0110 | 0110 | 0110 |
| +5 | 0101 | 0101 | 0101 |
| +4 | 0100 | 0100 | 0100 |
| +3 | 0011 | 0011 | 0011 |
| +2 | 0010 | 0010 | 0010 |
| +1 | 0001 | 0001 | 0001 |
| +0 | 0000 | 0000 | 0000 |
| −0 | — | 1111 | 1000 |
| −1 | 1111 | 1110 | 1001 |
| −2 | 1110 | 1101 | 1010 |
| −3 | 1101 | 1100 | 1011 |
| −4 | 1100 | 1011 | 1100 |
| −5 | 1011 | 1010 | 1101 |
| −6 | 1010 | 1001 | 1110 |
| −7 | 1001 | 1000 | 1111 |
| −8 | 1000 | — | — |

representation of negative numbers. The same procedures can be applied to the signed-1's-complement system by including the end-around carry as is done with unsigned numbers.

4.7 BINARY MULTIPLIER

Multiplication of binary numbers is performed in the same way as multiplication of decimal numbers. The multiplicand is multiplied by each bit of the multiplier, starting from the least significant bit. Each such multiplication forms a partial product. Successive partial products are shifted one position to the left. The final product is obtained from the sum of the partial products.

To see how a binary multiplier can be implemented with a combinational circuit, consider the multiplication of two 2-bit numbers as shown in Fig. 4.15. The multiplicand

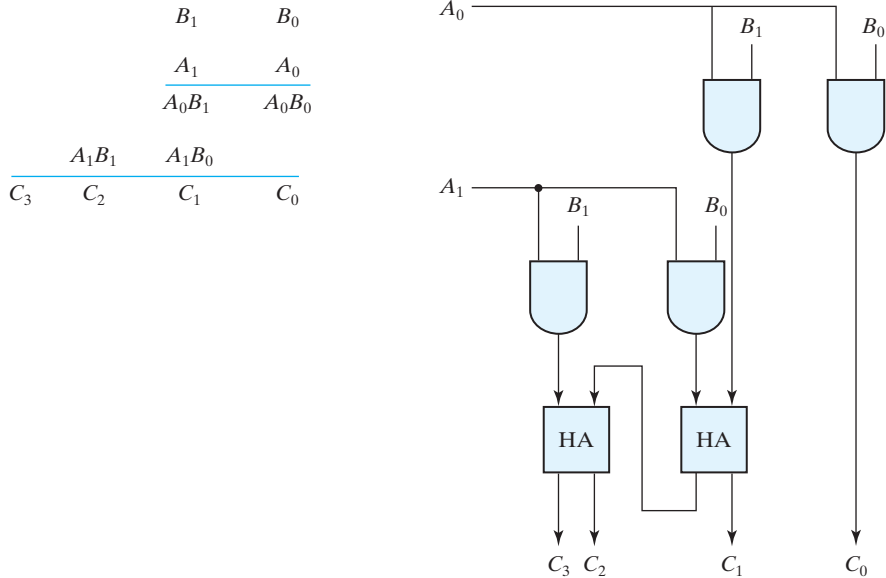


FIGURE 4.15
Two-bit by two-bit binary multiplier

bits are B_1 and B_0 , the multiplier bits are A_1 and A_0 , and the product is $C_3C_2C_1C_0$. The first partial product is formed by multiplying B_1B_0 by A_0 . The multiplication of two bits such as A_0 and B_0 produces a 1 if both bits are 1; otherwise, it produces a 0. This is identical to an AND operation. Therefore, the partial product can be implemented with AND gates as shown in the diagram. The second partial product is formed by multiplying B_1B_0 by A_1 and shifting one position to the left. The two partial products are added with two half-adder (HA) circuits. Usually, there are more bits in the partial products and it is necessary to use full adders to produce the sum of the partial products. Note that the least significant bit of the product does not have to go through an adder, since it is formed by the output of the first AND gate.

A combinational circuit binary multiplier with more bits can be constructed in a similar fashion. A bit of the multiplier is ANDed with each bit of the multiplicand in as many levels as there are bits in the multiplier. The binary output in each level of AND gates is added with the partial product of the previous level to form a new partial product. The last level produces the product. For J multiplier bits and K multiplicand bits, we need $(J \times K)$ AND gates and $(J - 1)$ K -bit adders to produce a product of $(J + K)$ bits.

As a second example, consider a multiplier circuit that multiplies a binary number represented by four bits by a number represented by three bits. Let the multiplicand be represented by $B_3B_2B_1B_0$ and the multiplier by $A_2A_1A_0$. Since $K = 4$ and $J = 3$, we need 12 AND gates and two 4-bit adders to produce a product of seven bits. The logic diagram of the multiplier is shown in Fig. 4.16.


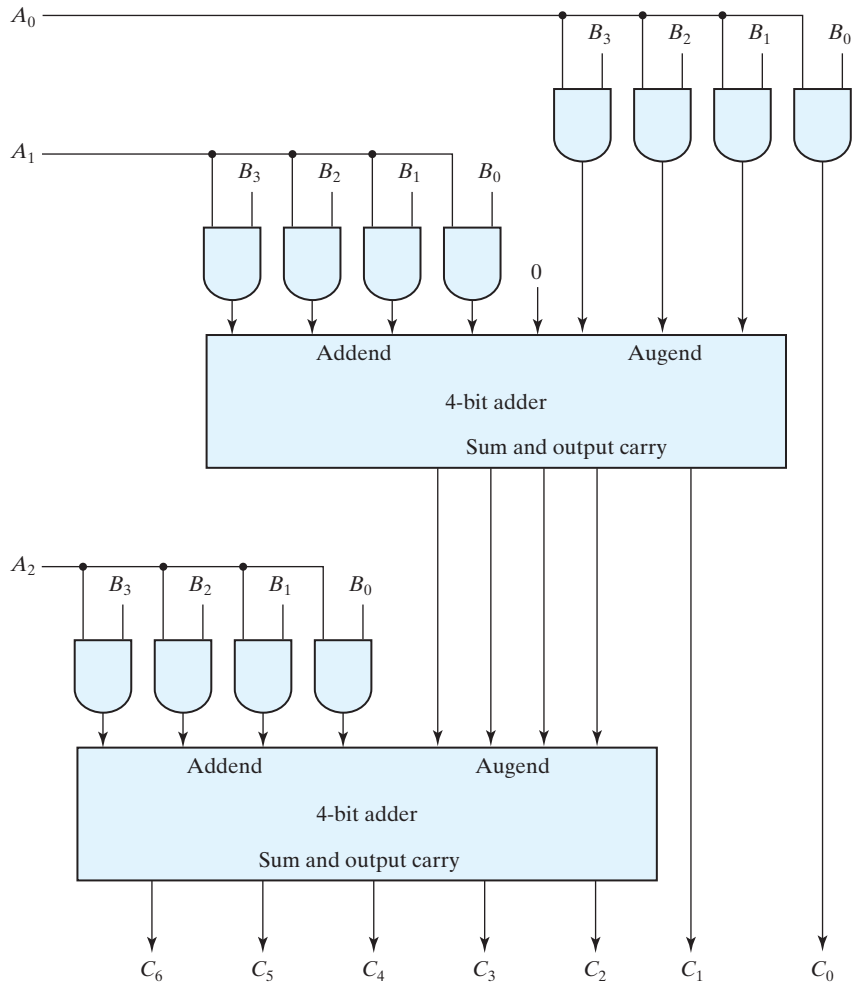



FIGURE 4.16
Four-bit by three-bit binary multiplier

Unsigned Multiplication


| | | | | X_3 Y_3 | X_2 Y_2 | X_1 Y_1 | X_0 Y_0 |
|----------|----------|----------|----------|----------------|----------------|----------------|----------------|
| | | | | X_3Y_0 | X_2Y_0 | X_1Y_0 | X_0Y_0 |
| | X_3Y_1 | | | X_2Y_1 | X_1Y_1 | X_0Y_1 | |
| | C_{12} | | | C_{11} | C_{10} | | |
| | C_{13} | S_{13} | | S_{12} | S_{11} | S_{10} | |
| | X_3Y_2 | X_2Y_2 | | X_1Y_2 | X_0Y_2 | | |
| | C_{22} | C_{21} | | C_{20} | | | |
| | C_{23} | S_{23} | S_{22} | S_{21} | S_{20} | | |
| | X_3Y_3 | X_2Y_3 | X_1Y_3 | X_0Y_3 | | | |
| | C_{32} | C_{31} | C_{30} | | | | |
| C_{33} | S_{33} | S_{32} | S_{31} | S_{30} | | | |
| P_7 | P_6 | P_5 | P_4 | P_3 | P_2 | P_1 | P_0 |

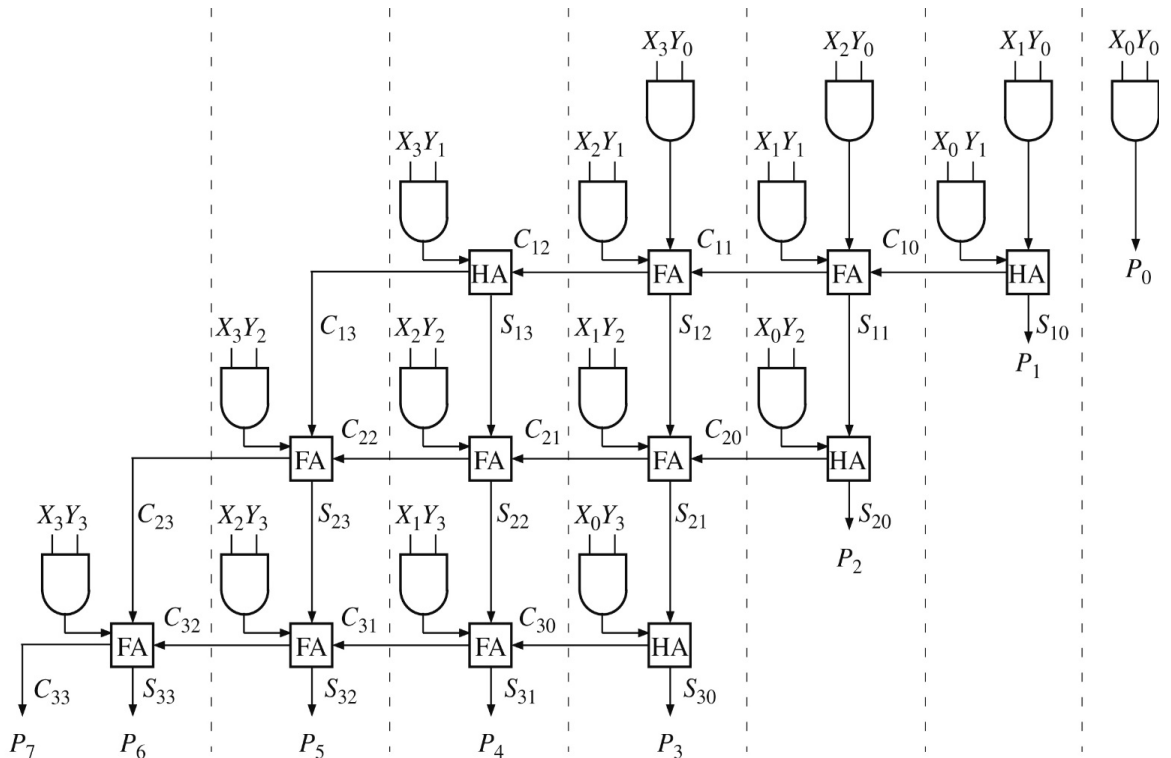

Unsigned Multiplication

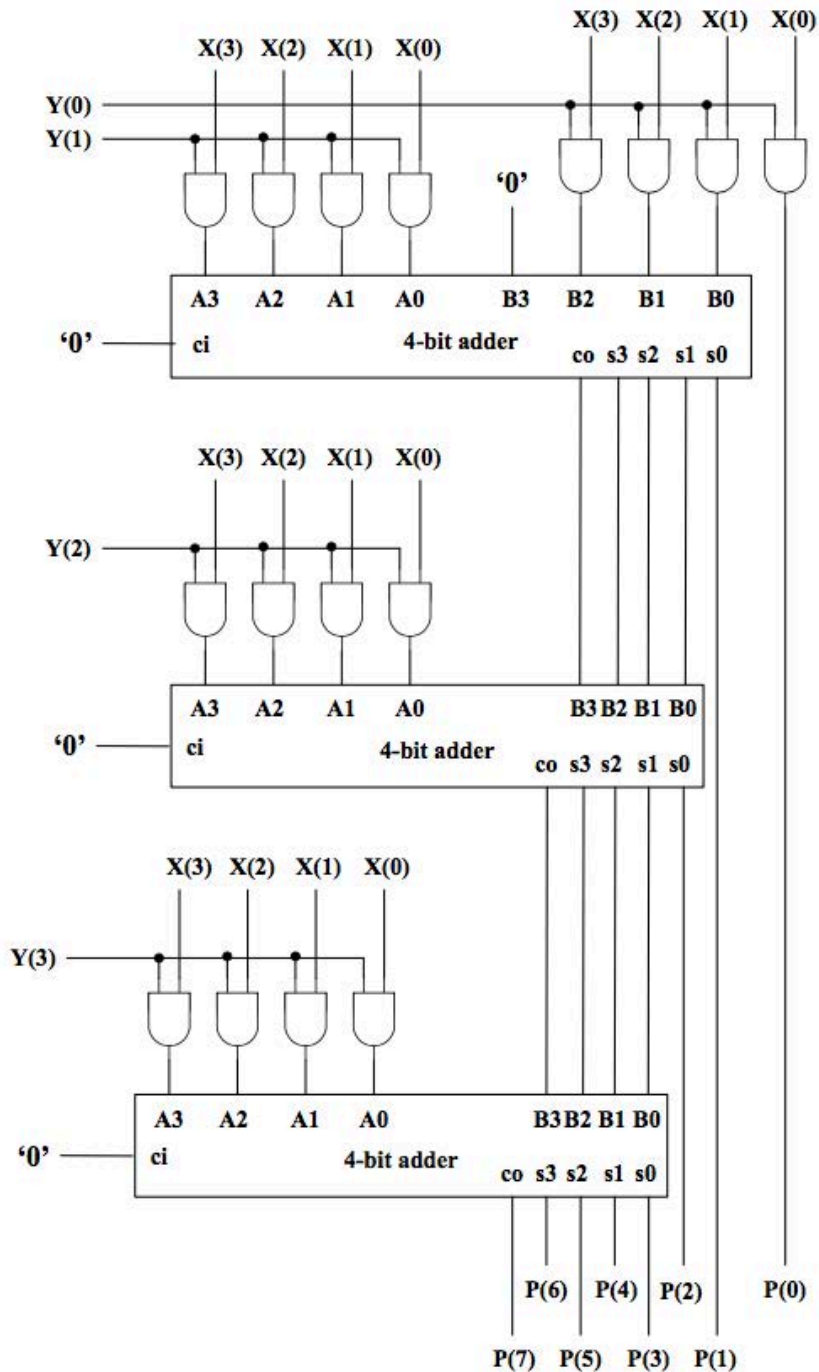

Signed Multiplication

 

$$(-3) * (-2)$$

(-3)

(-2)

$$\begin{array}{rcccc}
 & & & & \\
 & & & & \\
 * & \textcolor{red}{1} & 0 & 1 & (X) \\
 & \textcolor{red}{1} & 1 & 0 & (Y)
 \end{array}$$

0 0 0 0 0 0

$$Y_0 * X = 0$$

+ 1 1 1 0 1

$$2Y_1 * X = -6$$

- 1 1 0 1

$$4Y_2 * X = -12$$



(+6)

0 0 0 1 1 0

Signed Multiplication

$$\begin{array}{r}
 \begin{array}{cccc}
 X3 & X2 & X1 & X0 \\
 * & Y3 & Y2 & Y1 & Y0
 \end{array} \\
 \hline
 X3Y0 & X3Y0 & X3Y0 & X3Y0 & X3Y0 & X2Y0 & X1Y0 & X0Y0 \\
 + & X3Y1 & X3Y1 & X3Y1 & X3Y1 & X2Y1 & X1Y1 & X0Y1 \\
 + & X3Y2 & X3Y2 & X3Y2 & X2Y2 & X1Y2 & X0Y2 & \\
 - & X3Y3 & X3Y3 & X2Y3 & X1Y3 & X0Y3 & & \\
 \hline
 \end{array}$$

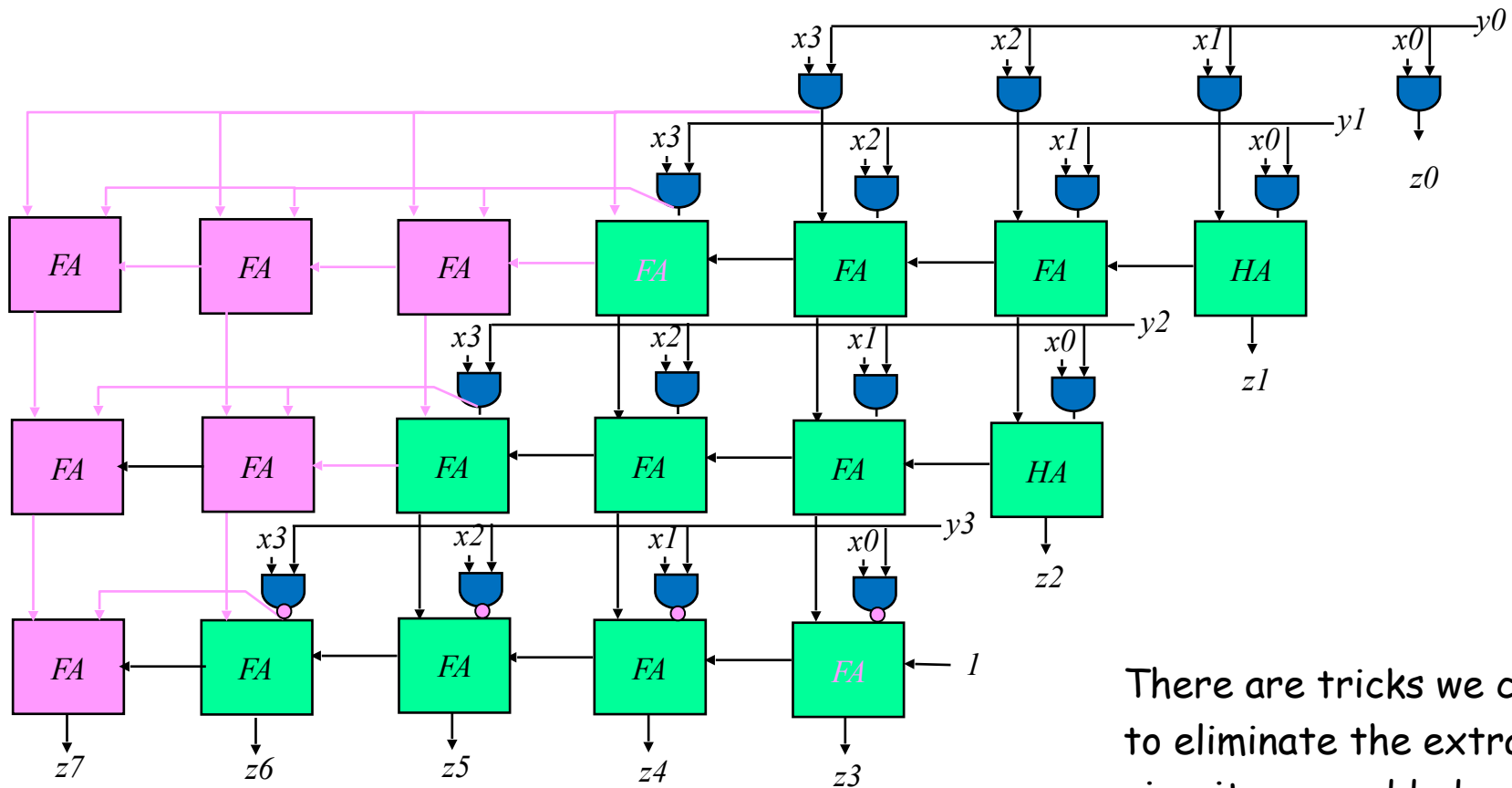 $z7 \quad z6 \quad z5 \quad z4 \quad z3 \quad z2 \quad z1 \quad z0$



There are tricks we can use to eliminate the extra circuitry we added...

(Baugh-Wooley Method)

Step 1: two's complement operands so high order bit is -2^{N-1} . Must sign extend partial products and **subtract** the last one

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & \textcolor{red}{x3} & x2 & x1 & x0 \\
 * & & & & \textcolor{red}{y3} & y2 & y1 & y0 \\
 \hline
 \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & x2y2 & x1y2 & x0y2 & \\
 - & \textcolor{red}{x3y3} & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & \\
 \hline
 & z7 & z6 & z5 & z4 & z3 & z2 & z1 & z0
 \end{array}
 \end{array}$$

Step 2: don't want all those extra additions, so add a carefully chosen constant, remembering to subtract it at the end. Convert subtraction into add of (complement + 1).

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 x3y0 & x3y0 & x3y0 & x3y0 & x3y0 & x2y0 & x1y0 & x0y0 \\
 + & & & & \textcolor{red}{1} & & & \\
 + & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & & \textcolor{red}{1} & & & & \\
 + & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & \textcolor{red}{x3y2} & x2y2 & x1y2 & x0y2 & \\
 + & & \textcolor{red}{1} & & & & & \\
 + & \textcolor{red}{x3y3} & \textcolor{red}{x3y3} & \textcolor{red}{x2y3} & \textcolor{red}{x1y3} & \textcolor{red}{x0y3} & & \\
 + & & & & & \textcolor{red}{1} & & \\
 + & & \textcolor{red}{1} & & & & & \\
 - & & \textcolor{red}{1} & \textcolor{red}{1} & \textcolor{red}{1} & \textcolor{red}{1} & &
 \end{array}
 \end{array}
 \left. \vphantom{\begin{array}{r} \dots \end{array}} \right\} -B = \sim B + 1$$

Step 3: add the ones to the partial products and propagate the carries. All the sign extension bits go away!

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & & & & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & \textcolor{red}{x2y2} & x1y2 & x0y2 & & & \\
 + & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & & \\
 + & & & & & & 1 & \\
 - & & 1 & 1 & 1 & 1 & &
 \end{array}
 \end{array}$$


Step 4: finish computing the constants...

$$\begin{array}{r}
 \begin{array}{ccccccccc}
 & & & & \textcolor{red}{x3y0} & x2y0 & x1y0 & x0y0 \\
 + & & & & \textcolor{red}{x3y1} & x2y1 & x1y1 & x0y1 \\
 + & & \textcolor{red}{x2y2} & x1y2 & x0y2 & & & \\
 + & \textcolor{red}{x3y3} & x2y3 & x1y3 & x0y3 & & & \\
 + & & & & & & 1 & \\
 + & 1 & & & & & & 1
 \end{array}
 \end{array}$$

Result: multiplying 2's complement operands takes just about same amount of hardware as multiplying unsigned operands!

Signed Multiplication
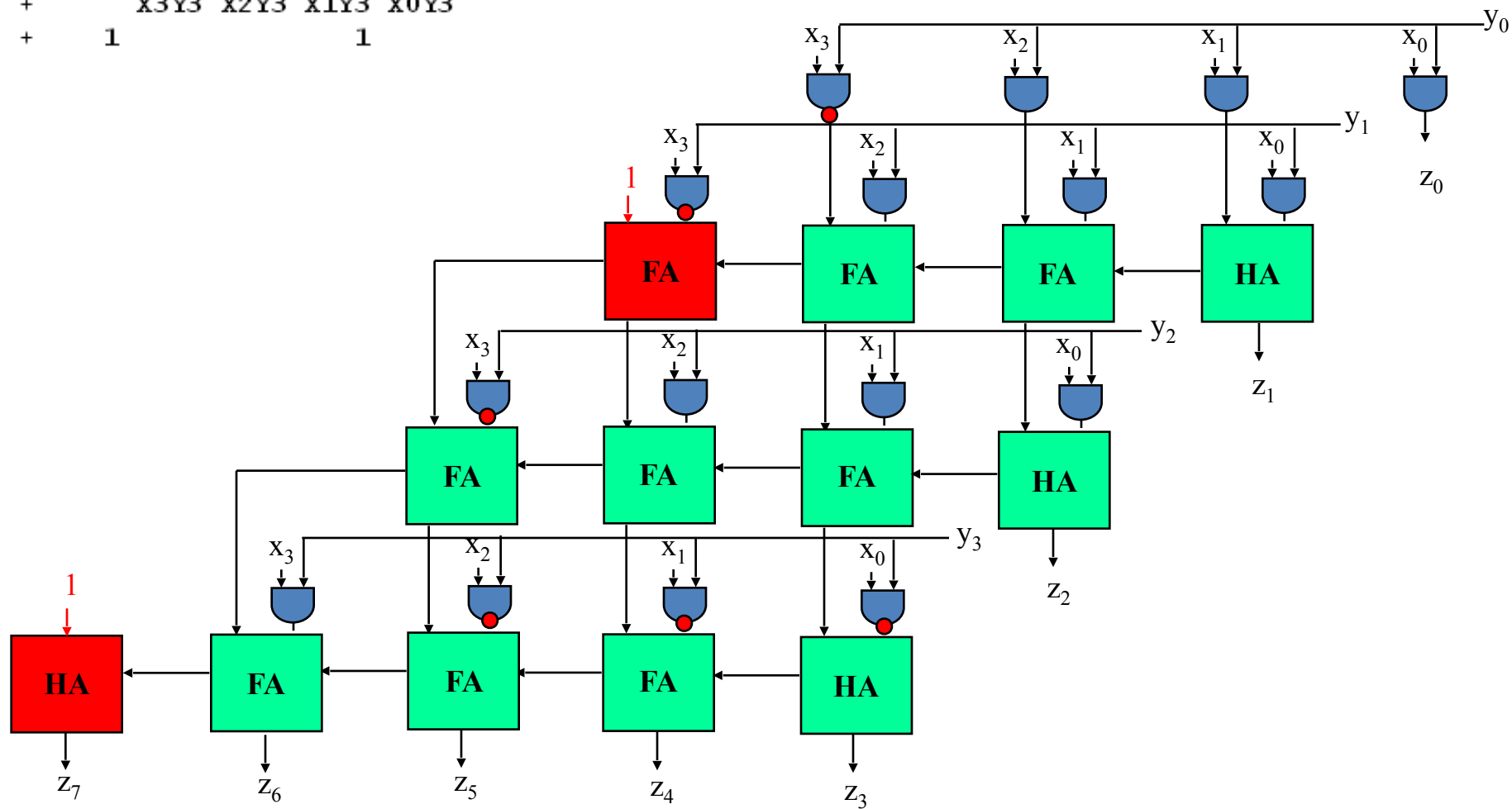
$$\begin{array}{rcccccccc}
& & & & & \overline{x_3y_0} & x_2y_0 & x_1y_0 & x_0y_0 \\
+ & & & & \overline{x_3y_1} & x_2y_1 & x_1y_1 & x_0y_1 & \\
+ & & \overline{x_2y_2} & \overline{x_1y_2} & \overline{x_0y_2} & & & & \\
+ & x_3y_3 & \overline{x_2y_3} & \overline{x_1y_3} & \overline{x_0y_3} & & & & \\
+ & 1 & & 1 & & & & &
\end{array}$$



Multiplication_4Bit

```
1  --Mohammad Niknam 951843189
2  library IEEE;
3  use IEEE.STD_LOGIC_1164.ALL;
4
5  entity Multiplication_4Bit is
6      port (
7          x: in  std_logic_vector (3 downto 0);
8          y: in  std_logic_vector (3 downto 0);
9          p: out std_logic_vector (7 downto 0));
10 end Multiplication_4Bit;
11
12 architecture structural of Multiplication_4Bit is
13     signal G0, G1, G2:  std_logic_vector (3 downto 0);
14     signal B0, B1, B2:  std_logic_vector (3 downto 0);
15     signal TMP: std_logic;
16
17     component ADDER_4BIT
18     port(IN1, IN2 : in std_logic_vector(3 downto 0) ;
19         CIN : in std_logic ;
20         COUT : out std_logic ;
21         SUM : out std_logic_vector(3 downto 0)) ;
22     end component;
23
24     component HF
25     port(A, B : in std_logic ;
26         S, C : out std_logic) ;
27     end component;
28
29 begin
30     G0 <= (not(x(3) and y(1)), x(2) and y(1), x(1) and y(1), x(0) and y(1));
31     G1 <= (not(x(3) and y(2)), x(2) and y(2), x(1) and y(2), x(0) and y(2));
32     G2 <= (x(3) and y(3), not(x(2) and y(3)), not(x(1) and y(3)), not(x(0) and y(3)));
33     B0 <= ('1', not(x(3) and y(0)), x(2) and y(0), x(1) and y(0));
34
35     ADDER_1: ADDER_4BIT
36     port map (
37         IN1 => G0,
38         IN2 => B0,
39         CIN => '0',
40         COUT => B1(3),
41         SUM(3) => B1(2),
42         SUM(2) => B1(1),
43         SUM(1) => B1(0),
44         SUM(0) => p(1) );
45
46     ADDER_2: ADDER_4BIT
47     port map (
48         IN1 => G1,
49         IN2 => B1,
50         CIN => '0',
51         COUT => B2(3),
52         SUM(3) => B2(2),
53         SUM(2) => B2(1),
54         SUM(1) => B2(0),
55         SUM(0) => p(2));
56
57     ADDER_3: ADDER_4BIT
58     port map (
59         IN1 => G2,
60         IN2 => B2,
61         CIN => '0',
62         COUT => TMP,
63         SUM => p(6 downto 3));
64
65     Half_Adder: HF
66     port map (
67         A => TMP,
68         B => '1',
69         S => p(7)
70     );
71
72     p(0) <= x(0) and y(0);
73 end structural;
```

Multiplication_4Bit

The screenshot displays a VHDL development environment with the following components:

- Design Window:** Shows the project hierarchy. The selected entity is `Multiplication_4Bit_TB - behavior (Multiplication_4Bit_TB.vhd)`.
- Processes Window:** Lists the simulation processes. The `Behavioral Check Syntax` process is highlighted, indicating it has completed successfully.
- VHDL Code Editor:** Contains the source code for `Multiplication_4Bit.vhd`. The code defines a 4-bit multiplier using a component `ADDER_4BIT` and logic for generating carry bits `G0`, `G1`, `G2`, and `B0`.
- Console Window:** Displays the output of the `Behavioral Check Syntax` process, showing that the VHDL files were parsed successfully into the `isim_temp` library.

```
22 port (IN1, IN2 : in std_logic_vector(3 downto 0) ;
23       CIN : in std_logic ;
24       COUT : out std_logic ;
25       SUM : out std_logic_vector(3 downto 0)) ;
26 end component;
27
28
29 component HF
30 port (A, B : in std_logic ;
31       S, C : out std_logic) ;
32 end component;
33
34
35
36 begin
37   G0 <= (not(x(3) and y(1)), x(2) and y(1), x(1) and y(1), x(0) and y(1));
38   G1 <= (not(x(3) and y(2)), x(2) and y(2), x(1) and y(2), x(0) and y(2));
39   G2 <= (x(3) and y(3), not(x(2) and y(3)), not(x(1) and y(3)), not(x(0) and y(3)));
40   B0 <= ('1', not(x(3) and y(0)), x(2) and y(0), x(1) and y(0));
41
42   ADDER_1: ADDER_4BIT
43     port map (
44       IN1 => G0,
45       IN2 => B0,
46       CIN => '0',
47       COUT => B1(3),
48       SUM(3) => B1(2),
49       SUM(2) => B1(1),
50       SUM(1) => B1(0),
51       SUM(0) => p(1)
52     );
```

Console Output:

```
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/./Practices/Project ADDER_4BIT/FULL_ADDER.vhd" into library isim_temp
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/ADDER_4BIT.vhd" into library isim_temp
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/Multiplication_4Bit.vhd" into library isim_temp
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/Multiplication_4Bit_TB.vhd" into library isim_temp

Process "Behavioral Check Syntax" completed successfully
```

Multiplication_4Bit_TB

```
1  --Mohammad Niknam 951843189
2
3  librarLIBRARY ieee;
4  USE ieee.std_logic_1164.ALL;
5  use ieee.numeric_std.all;
6
7  ENTITY Multiplication_4Bit_TB IS
8  END Multiplication_4Bit_TB;
9
10 ARCHITECTURE behavior OF Multiplication_4Bit_TB IS
11
12
13     COMPONENT Multiplication_4Bit
14     PORT(
15         x : IN  std_logic_vector(3 downto 0);
16         y : IN  std_logic_vector(3 downto 0);
17         p : OUT std_logic_vector(7 downto 0)
18     );
19     END COMPONENT;
20
21
22     --Inputs
23     signal x : std_logic_vector(3 downto 0) := (others => '0');
24     signal y : std_logic_vector(3 downto 0) := (others => '0');
25
26     --Outputs
27     signal p : std_logic_vector(7 downto 0);
28
29
30 BEGIN
31
32     uut: Multiplication_4Bit PORT MAP (
33         x => x,
34         y => y,
35         p => p
36     );
37
38     stim_proc:process
39     begin
40         for i in 0 to 15 loop
41             x <= std_logic_vector(to_unsigned(i, x'length));
42             for j in 0 to 15 loop
43                 y <= std_logic_vector(to_unsigned(j, y'length));
44                 wait for 10 ns;
45             end loop;
46         end loop;
47         wait;
48     end process;
49
50 END;
```

Multiplication_4Bit_TB

The screenshot displays the ISE IDE interface for a VHDL project. The main Text Editor window shows the content of `Multiplication_4Bit_TB.vhd`. The left pane shows the Hierarchy tree with `Multiplication_4Bit_TB - behavior (Multiplication_4Bit_TB)` selected. The bottom pane shows the Console with messages about parsing VHD files and successful behavioral check syntax.

```
19
20 --Inputs
21 signal x : std_logic_vector(3 downto 0) := (others => '0');
22 signal y : std_logic_vector(3 downto 0) := (others => '0');
23
24 --Outputs
25 signal p : std_logic_vector(7 downto 0);
26
27
28 BEGIN
29
30 uut: Multiplication_4Bit PORT MAP (
31     x => x,
32     y => y,
33     p => p
34 );
35
36 stim_proc:process
37 begin
38     for i in 0 to 15 loop
39         x <= std_logic_vector(to_unsigned(i, x'length));
40         for j in 0 to 15 loop
41             y <= std_logic_vector(to_unsigned(j, y'length));
42             wait for 10 ns;
43         end loop;
44     end loop;
45     wait;
46 end process;
47
48 END;
```


Console Output:

```
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/Multiplication_4Bit.vhd" into library isim_temp
Parsing VHDL file "E:/Videos/Learning/Electrical Engineering/JSU/#Term10/VHDL/VHDL project/Multiplication_4Bit/Multiplication_4Bit_TB.vhd" into library isim_temp


Process "Behavioral Check Syntax" completed successfully

Started : "Launching ISE Text Editor to edit Multiplication_4Bit_TB.vhd".
```


Simulation:

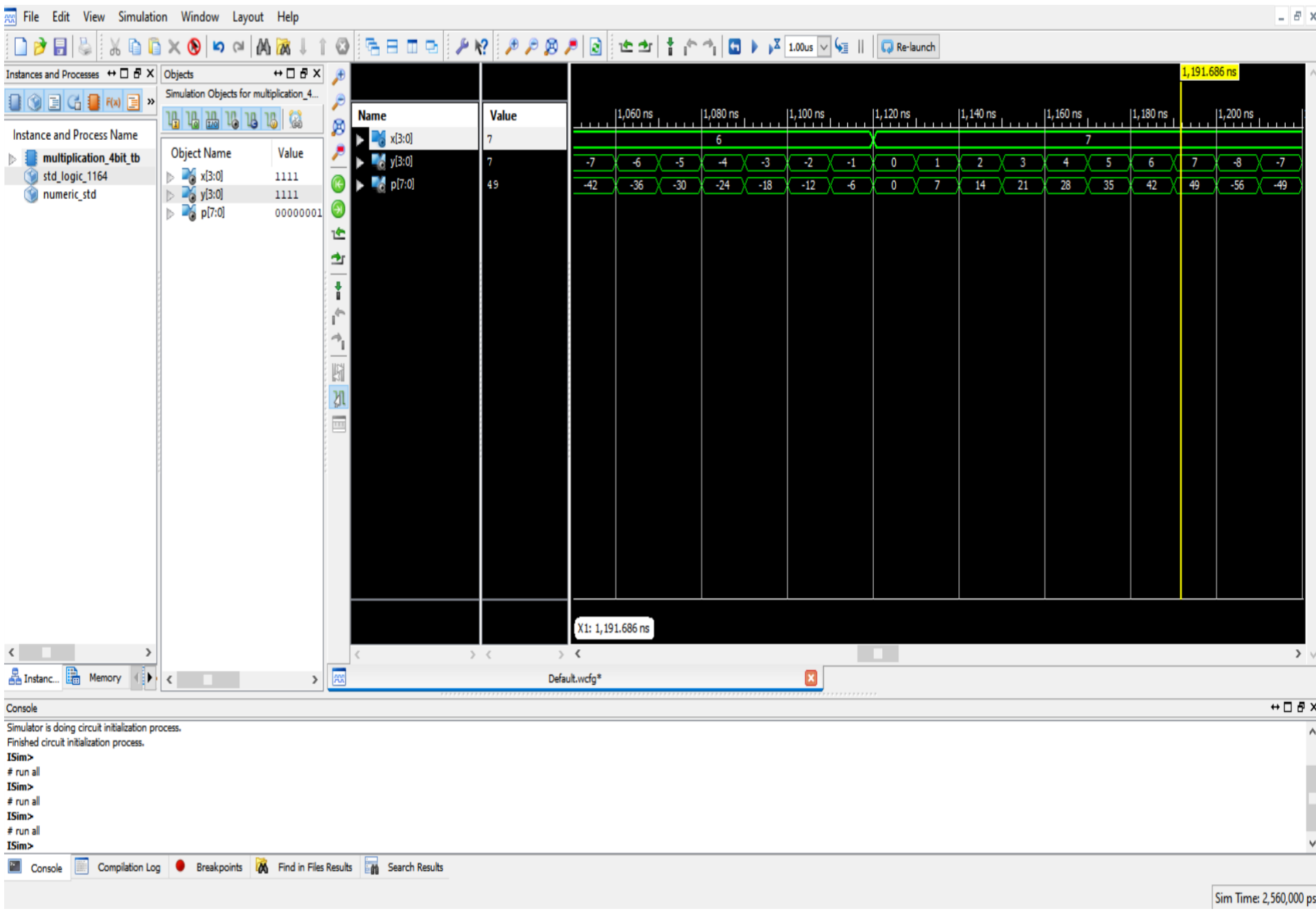

Simulation:

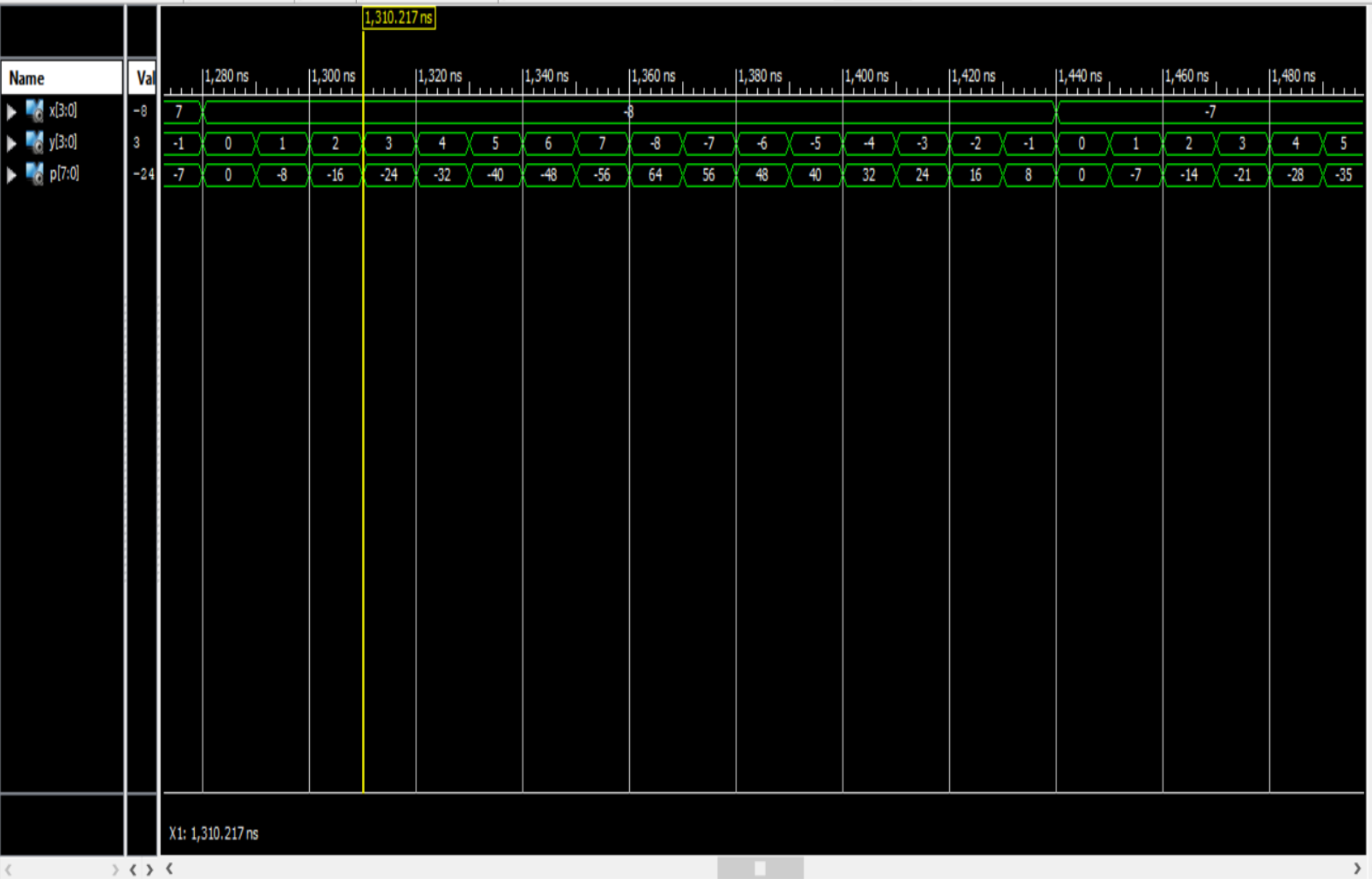

Synthesize & RTL Schematic

